

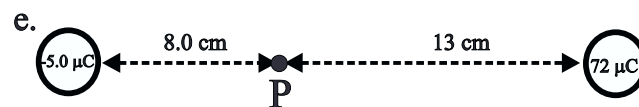
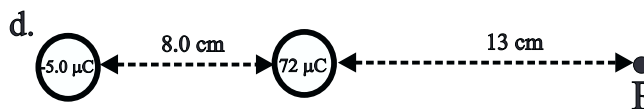
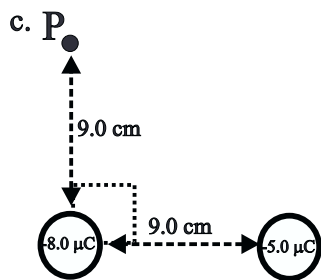
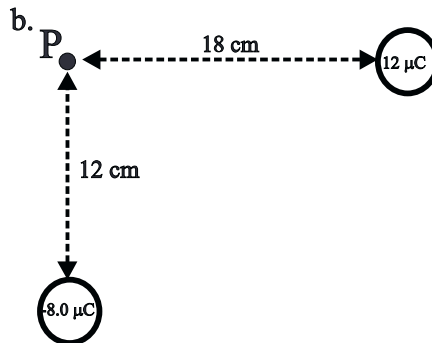


ELECTROSTATIC POTENTIAL ENERGY

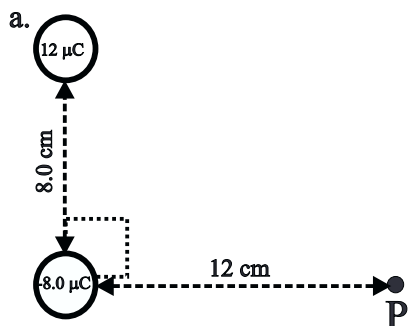6. What will be the electrostatic potential of a point **P** which is both 12.0 cm from a 25.0 μC charge and 6.0 cm from a 50 μC charge?
7. Determine the **electrostatic potential** at point **P** in each of the following diagrams.



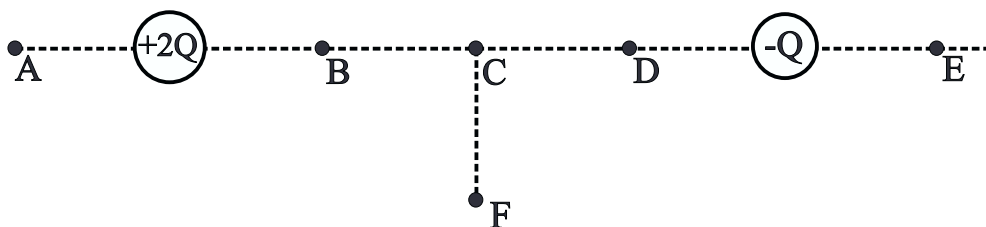8. Suppose that in each diagram above a 7.00 μC charge is to be moved from **infinity** to point **X**. In each case above, determine how much **work** would be required to place the 7.00 μC charge at point **X**.
9. What will be the **electrostatic potential energy** of each set of charges above? [including the 7.0 μC charge!]
10. Each of the following questions refers to the diagram below.



- a. At which point in the above diagram will the **electric field strength** be the **greatest**?
- b. At which point in the above diagram will the **electrostatic potential** be the **greatest**?
- c. At which point in the above diagram will the **electric field strength** be the **weakest**?
- d. At which point in the above diagram will the **electrostatic potential** be the **least**?

ANSWERS TO THE OPPOSITE SIDE: 1a. 37.5 μF b. 2700 μC 2. 16 μF 3. 1260 μC 4. 30,000 μC											
5. 0.015 μF	6. 0.22 μF	7. 20.3 μF	8. 238 m^2	9. 400 μF	10. 155 μF	11. 500 μF	12. 0.030 J				
13. 14.4 J	14. 144 Volts	15. 161 μF									

PHYSICS HOMEWORK #146

ELECTROSTATIC POTENTIAL

CAPACITORS & CAPACITANCE

- A given capacitor is rated to store 450 μC of charge whenever a potential difference of 12.0 Volts is applied.
 - What is the capacitance of this capacitor?
 - How much charge will this capacitor store when a potential difference of 72.0 Volts is applied?

$$C = \frac{q}{V} = \frac{\epsilon \cdot A}{d} \quad \epsilon = \epsilon_o \cdot K \quad \epsilon_o = 8.85 \cdot 10^{-12} \cdot \frac{\text{Farad}}{\text{m}}$$


- What is the capacitance of capacitor which can store 720 μC of charge whenever a potential difference of 45.0 Volts is applied?
- How much charge can be stored in a capacitor rated at 210 μF , if a potential difference of 6.00 Volts is applied?
- How much charge can be stored in a 2000 μF capacitor when a potential difference of 15.0 Volts is applied?

<u>DIELECTRIC MATERIAL</u>	<u>DIELECTRIC CONSTANT K</u>
AIR	1.0
PARAFFIN	2.2
POLYETHYLENE	2.3
POLYSTYRENE	2.5
HARD RUBBER	2.8
MICA	6.0
GLASS	8.0

- A parallel plate capacitor is made of two parallel plates, each of which has an area of 2.0 m^2 , and which are separated by 1.20 mm of air. What is the capacitance of this capacitor?
- What will be the capacitance of a parallel plate capacitor which is made from two parallel plates, each with an area of 3.5 m^2 , which are separated by 0.85 mm of mica ?
- What will be the capacitance of a parallel plate capacitor consisting of two two parallel plates, each of which has an area of 13.3 m^2 , which are separated by 0.0145 mm of polystyrene?
- A parallel plate capacitor is to be made from two conducting plates separated by 0.022 m of polyethylene. This capacitor is to have a total capacitance of 220 μF . What should the area of each plate of this capacitor be?
- What will be the total capacitance if a 250 μF capacitor is connected in parallel with a 150 μF capacitor?
- What will be the total capacitance if a 240 μF capacitor is connected in series with a 440 μF capacitor?

<p>Series</p> $\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_t}$ <p>Parallel</p> $C_1 + C_2 = C_t$ <p>Energy</p> $U = \frac{1}{2} \cdot C \cdot V^2$
--

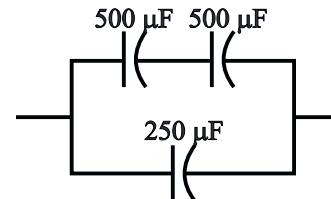- What will be the total capacitance if two 500 μF capacitors are connected in series with each other but which are connected in parallel with a 250 μF capacitor? See diagram at the right!
- How much energy will be stored in a 420 μF capacitor to which a potential difference of $V = 12.0$ Volts has been applied?




- How much energy would be stored in a 2000 μF capacitor attached to a 120 Volt power supply?
- A capacitor is rated at 1200 μF . What potential difference should be applied to this capacitor so that the energy stored in this capacitor is 12.4 Joules?
- What will be the total capacitance if a 350 μF , a 520 μF and a 700 μF capacitor are all connected in series?

Answers to opposite side: 6. 9,400,000 Volts 7a. 1.5×10^5 Volts b. 0.0 Volts c. -1.15×10^6 Volts d. 4.77×10^6 Volts											
7e. 4.42×10^6 Volts 8a. 1.05 J b. 0.0 J c. -8.08 J d. 33.4 J e. 30.9 J 9a. -9.75 J b. -3.99 J c. -4.08 J											
9d. -7.10 J e. 15.5 J 10a. B b. A c. E d. E											

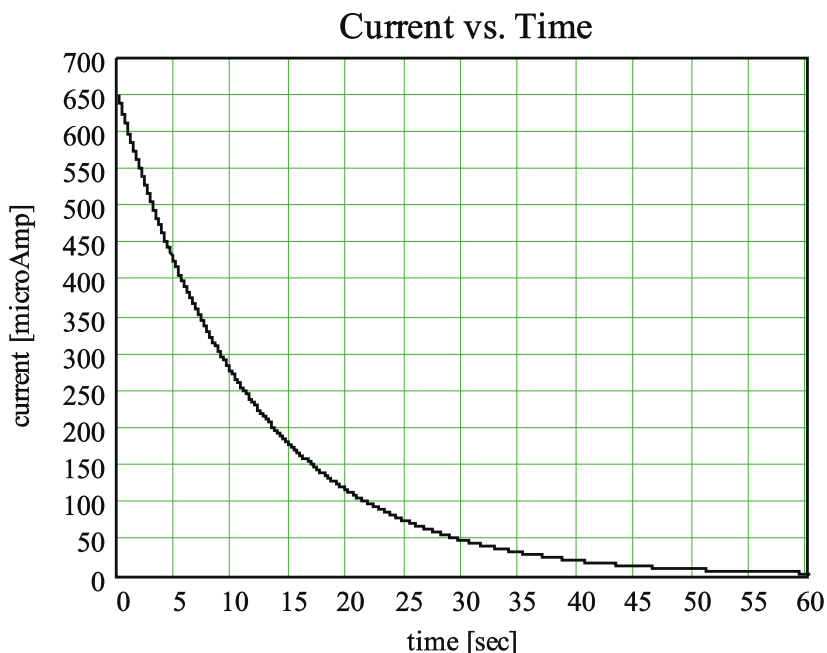16. A capacitor with a capacitance C is attached to a power supply which has a potential V and is then fully charged. This capacitor is then attached to a simple series circuit consisting of a galvanometer and a $13,000 \Omega$ resistor. The graph to the right represents the current flowing out of this capacitor as a function of time through the galvanometer.

- What was the initial current flowing out of the capacitor?
- What was the initial voltage across the capacitor?
- What is the time constant for this circuit?
- Write an equation describing the current flowing out of this circuit as a function of time?
- Using the equation derived in d above predict the current flowing out of this capacitor after $t = 30$ seconds and compare to the value on the graph.
- What was the total charge contained in this capacitor?
- What is the capacitance of this capacitor?
- How much charge will be stored in this capacitor after $t = 20$ seconds?
- What will be the current flowing out of this capacitor after $t = 85$ seconds?



17. A capacitor, which has a capacitance of $470 \mu\text{F}$, is attached to a 6.00 Volt battery and is fully charged. This capacitor is then removed from the battery and is attached in series to a 1500Ω resistor.

- What is the time constant for this circuit?
- What will be the total charge stored in this capacitor?
- What will be the initial current flowing through this circuit?
- What will be the current flowing through this circuit after 1.5 seconds?
- How long will it take for the current flowing in this circuit to fall to 1% of its initial value?

18. A $220 \mu\text{F}$ capacitor is charged up by a 12.0 Volt battery.

- What will be the charge stored on this capacitor after being charged up?

This capacitor is then attached to a second capacitor, which is initially uncharged and has a capacitance of $470 \mu\text{F}$.

- What will be the total charge stored on both of these capacitors after being attached together?
- What will be the charge stored on each of these capacitors after being attached together?
- What will be the potential difference across each of these capacitors after being attached together?

ANSWERS TO THE OPPOSITE SIDE:

19a.. $5000 \mu\text{C}$, $19,800 \mu\text{C}$ b. $24,800 \mu\text{C}$ c. $7750 \mu\text{C}$, $17,050 \mu\text{C}$ d. 7.75 Volts e. $14,800 \mu\text{C}$ f. $4625 \mu\text{C}$,
 19f. $10,175 \mu\text{C}$ g. 4.625 Volts 20a. $3300 \mu\text{C}$, $24,750 \mu\text{C}$ b. $28,050 \mu\text{C}$ c. $7010 \mu\text{C}$, $21,040 \mu\text{C}$
 20d. 12.75 Volts e. $21,450 \mu\text{C}$ f. $5360 \mu\text{C}$, $16,100 \mu\text{C}$ g. 9.75 Volts 21a. $2.30 \mu\text{F}$ b. $27.6 \mu\text{C}$ c. $166 \mu\text{J}$
 21d. $13.8 \mu\text{F}$ e. $166 \mu\text{C}$ f. $994 \mu\text{J}$ g. $828 \mu\text{J}$ 22. 48.0 C